

4-3 Find the voltage gain v_o/v_s and current gain i_o/i_x in Figure P4-3 for $g = 2 \times 10^{-3}$ S. For $v_s = 5$ V, find the power supplied by the input voltage source and the power delivered to the 2-k Ω load resistor.

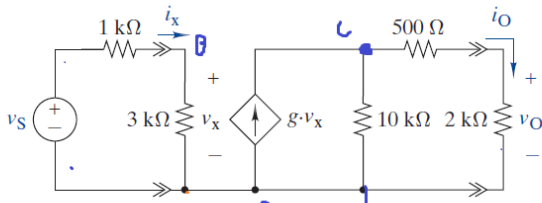


FIGURE P4-3

1ος τρόπος

Thevenin στην εξαρτημένη: μπορείς γιατί δεν εξαφανίζεται η εξάρτηση

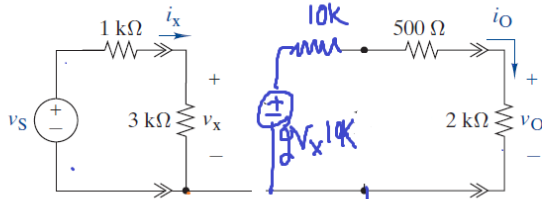


FIGURE P4-3

Διαιρέτης τάσης

$$v_o = g v_x \cdot 10k \cdot \frac{2k}{10k + 500 + 2k} = g v_x \cdot \frac{8 \cdot 10^3}{12.5k}$$

$$= g \cdot \frac{3}{4} \cdot v_s \cdot \frac{8}{5} \cdot 10^3 \Rightarrow \frac{v_o}{v_s} = g \cdot \frac{6 \cdot 10^3}{5} \frac{V}{V} = \frac{12}{5} \frac{V}{V}$$

2ος τρόπος: διαιρέτης ρεύματος πάνω στον κόμβο C

$$i_o = g v_x \cdot \frac{10k}{10k + 500 + 2k} \quad I_2 = \pm \frac{R_1}{R_1 + R_2}$$



$$v_o = i_o \cdot 2k = g v_x \cdot \frac{20 \cdot 10^3}{12.5} = g v_x \cdot \frac{8 \cdot 10^3}{5} \dots$$

$$v_o = g v_x \cdot \frac{8 \cdot 10^3}{5} \Rightarrow i_o \cdot 2k = g v_x \cdot \frac{8 \cdot 10^3}{5} \Rightarrow \frac{i_o}{i_x} = g \cdot \frac{12 \cdot 10^3}{5} =$$

$$= \frac{2 \cdot 10^{-3} \cdot 12 \cdot 10^3}{5} = \frac{24}{5} \frac{A}{A}$$

$$P_s = v_s \cdot i_x = v_s \cdot \frac{v_s}{(4/3)k} = \frac{25 \cdot 10^{-3}}{4} = 6.25 \text{ mW}$$


(4/3)k ← V^2/R

$$P_o = v_o \cdot i_o = \frac{v_o}{v_s} \cdot v_s \cdot \frac{i_o}{i_x} \cdot i_x = \frac{v_o \cdot i_o}{v_s \cdot i_x} \cdot v_s \cdot \frac{v_s}{4k} =$$

$$= \frac{12}{5} \cdot \frac{24}{5} \cdot \frac{5}{8} \cdot \frac{5}{4 \cdot 10^3} = 72 \text{ mW}$$

4-8 (a) Find an expression for the gain i_O/v_S in Figure P4-8 in terms of R_X .

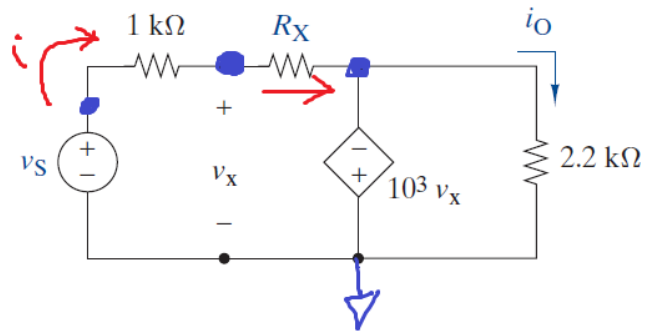(b) Select a value for R_X so that the gain is -0.227 .



$$i_O = -\frac{V_S}{2.2} \left(\frac{R_X}{R_X + 1001 \cdot 10^3} \right)$$

$$i_O = -\frac{10^3 V_X}{2.2 \text{ k}\Omega} = -\frac{V_X}{2.2} \quad (1)$$

$$i = \frac{V_X + 10^3 V_X}{R_X} = \frac{1001 V_X}{R_X} \quad (2)$$

$$V_S - \frac{1001 V_X \cdot 1 \text{ k}}{R_X} = V_X \Rightarrow V_X \left(1 + \frac{1001 \cdot 10^3}{R_X} \right) = V_S \Rightarrow V_X \left(\frac{R_X + 1001 \cdot 10^3}{R_X} \right) = V_S \Rightarrow$$

$$\Rightarrow V_X = \frac{R_X}{R_X + 1001 \cdot 10^3} V_S \quad (3)$$

4-9 Find an expression for the voltage gain v_o/v_s in Figure P4-9.

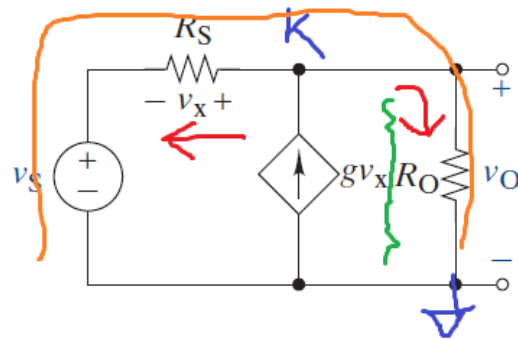


FIGURE P4-9

Νόμος Ρευμάτων Kirchhoff, όπου τα
ρεύματα γράφονται σαν τάσεις:
Μέθοδος Κόμβων Nodal Analysis

$$g v_x = \frac{V_x}{R_s} + \frac{V_o}{R_o} \Rightarrow V_x \left(g - \frac{1}{R_s} \right) = \frac{V_o}{R_o} \Rightarrow V_x \left(\frac{g R_s - 1}{R_s} \right) = \frac{V_o}{R_o} \quad (1)$$

$$\underbrace{V_s + V_x - V_o = 0} \Rightarrow \underbrace{V_x = V_o - V_s} \quad (2) \quad \downarrow \quad (V_o - V_s) \left(\frac{g R_s - 1}{R_s} \right) = \frac{V_o}{R_o} \Rightarrow$$

$$\Rightarrow \underline{R_o} (V_o - V_s) (g R_s - 1) = R_s V_o \Rightarrow V_o [R_o (g R_s - 1) - R_s] = R_o V_s (g R_s - 1) \Rightarrow$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{R_o \cdot (g R_s - 1)}{[R_o (g R_s - 1) - R_s]}$$

4-10 (a) Find an expression for the voltage gain v_O/v_S in Figure P4-10.

(b) Let $R_S = 10 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$ and $\mu = 100$. Find the voltage gain v_O/v_S as a function of R_F . What is the voltage gain when R_F is an open circuit, a short circuit, and for $R_F = 100 \Omega$?

(c) Simulate the circuit in OrCAD by varying R_F from 1Ω to $10 \text{ M}\Omega$. Read your output $R_F = 100 \Omega$. How does your answer compare with part (b)?

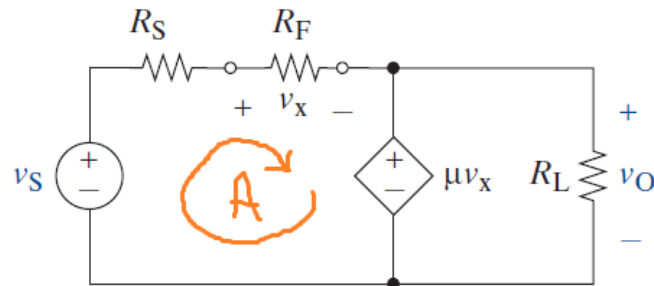


FIGURE P4-10

$$\frac{V_O}{V_S} = \mu \cdot \frac{R_F}{R_S + (\mu + 1)R_F}$$

$$V_O = \mu V_X \quad (1)$$

$$V_S - \frac{V_X R_S}{R_F} - V_X = \mu V_X \Leftrightarrow$$

$$\Leftrightarrow V_S \cdot R_F = V_X (R_S + R_F + \mu R_F) \Leftrightarrow$$

$$\Rightarrow V_X = \frac{V_S \cdot R_F}{R_S + (\mu + 1)R_F}$$

$$A_v \quad R_F \rightarrow \infty$$

$$\lim_{R_F \rightarrow \infty} \frac{V_O}{V_S} = \frac{\mu}{\mu + 1}$$

$$A_v \quad R_F \rightarrow 0$$

$$\lim_{R_F \rightarrow 0} \frac{V_O}{V_S} = 0$$

4-17 Find the Norton Equivalent circuit seen by the load in Figure P4-17.

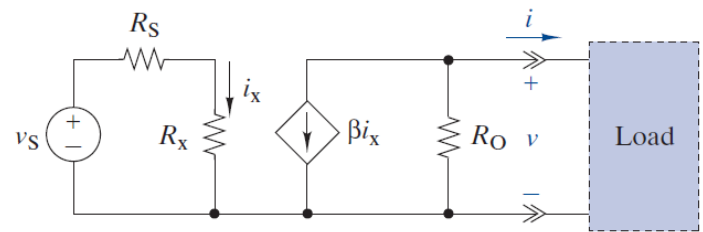


FIGURE P4-17

Κατευθείαν Norton:
βραχυκυκλώνεις τους ακροδέκτες και
ψάχνεις το ρεύμα βραχυκύκλωσης

$$i = \beta i_x$$


$$i_x = \frac{V_s}{R_s + R_x}$$

$$i = \beta \frac{V_s}{R_s + R_x}$$

$$i = \frac{\beta i_x R_o}{R_o} = \beta i_x$$

$$R_n = R_{th} = V_t / i_t$$

βραχυκυκλώσαμε
τη V_s .

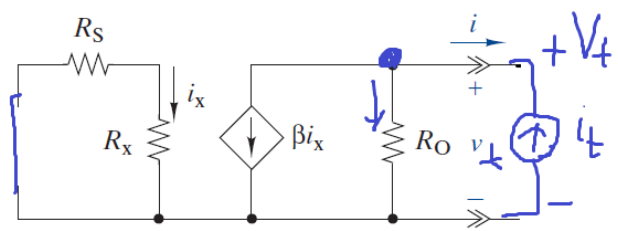

βάζουμε δοκιμαστική πηγή

$$i_t = \frac{V_t}{R_o} + \beta i_x = \frac{V_t}{R_o} + \beta \cdot 0 \Rightarrow R_n = \frac{V_t}{i_t} = R_o$$

δεν υπάρχει ρεύμα

